



**CSE-2103**

**Computer Architecture**



# **Lecture – 1, 2**

# Text Books

- ***Computer Architecture and Organization***  
Hayes J.P., McGraw-Hill.
- ***Computer organization and design: The hardware/software interface***  
Patterson D.A., Hennessy J.L., Morgan Kaufmann.



# Reference Book


- ***Computer Architecture: A Quantitative Approach***  
Patterson D.A., Hennessy J.L., Morgan Kaufmann.



# Fixed-Point Arithmetic

- Addition
- Subtraction
- Multiplication
- Division

# Half Adder

 


$X_0 Y_0$	$S_0 C_0$
0 0	0 0
0 1	1 0
1 0	1 0
1 1	1 1

$$S_0 = X_0 \oplus Y_0$$

$$C_0 = X_0 Y_0$$

# Full Adder


 


Inputs			Outputs	
$x_0$	$y_0$	$c_{-1}$	$c_0$	$s_0$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S_0 = X_0 \oplus Y_0 \oplus C_{-1}$$


$$C_0 = X_0 Y_0 + X_0 C_{-1} + Y_0 C_{-1}$$

# Full Adder

 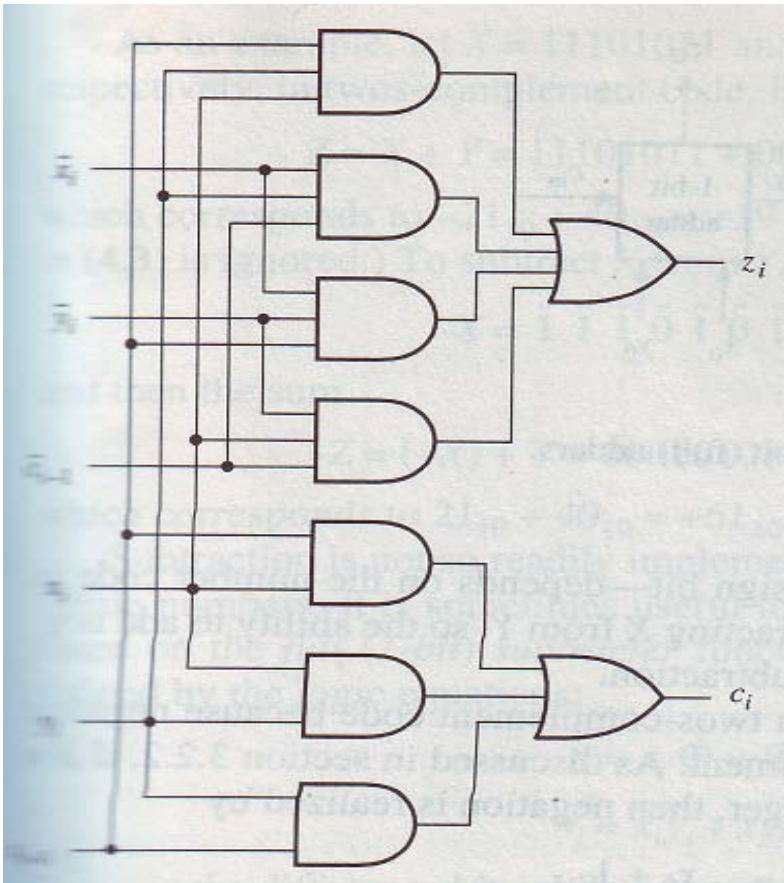




# Serial Binary Adder

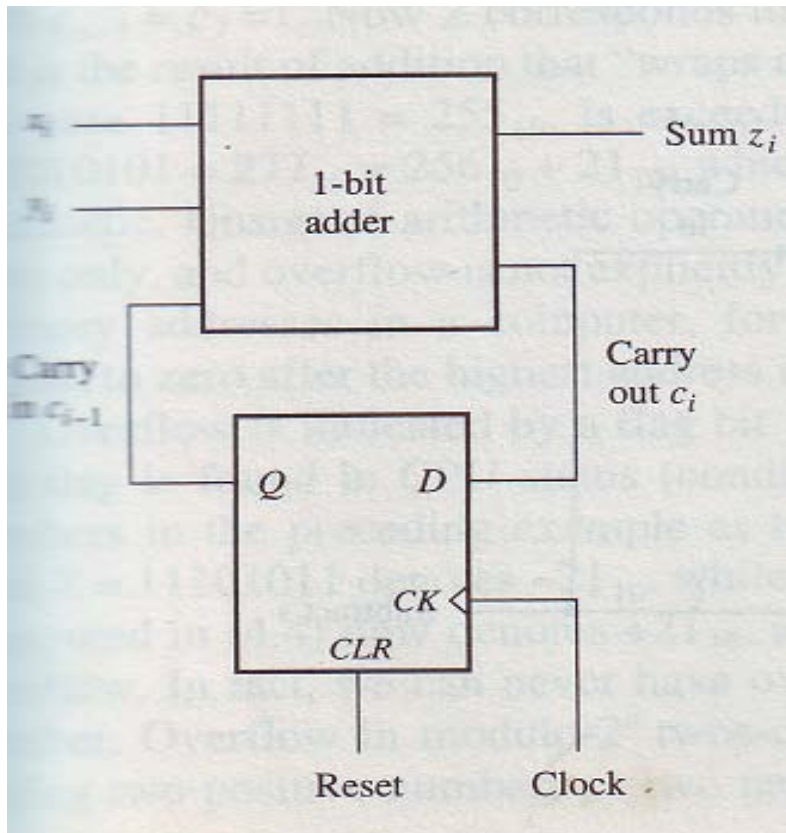


- Least expensive circuit in terms of hardware cost.
- It adds the numbers bit by bit and so requires  $n$  clock cycle to compute the sum of two  $n$ -bit numbers.
- Circuit size independent of  $n$ .

# Ripple Carry Adder

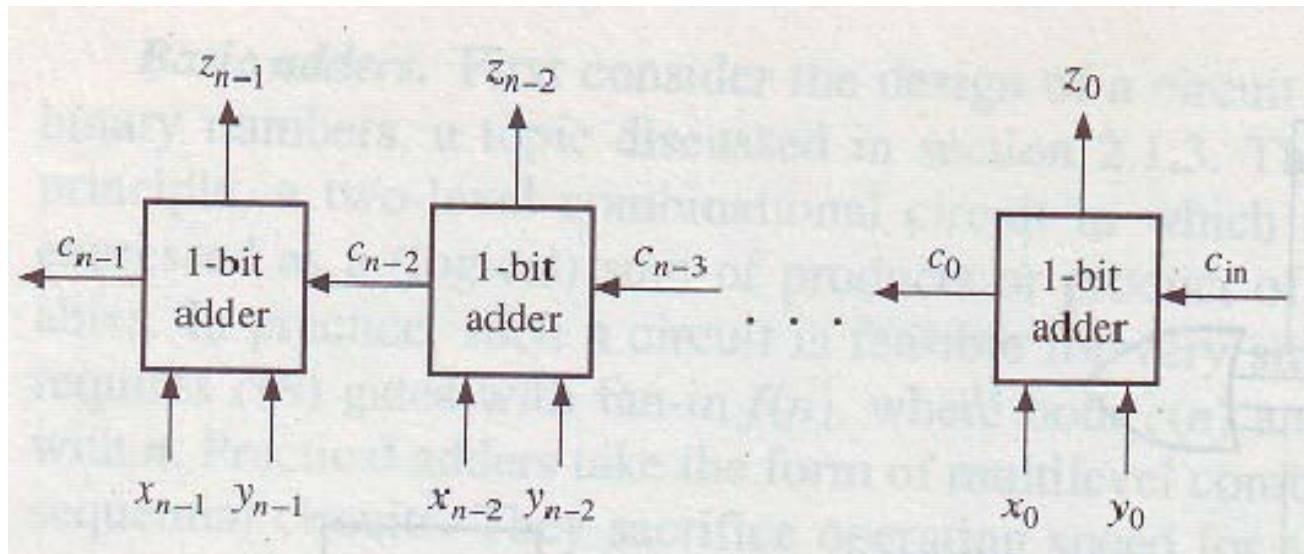

- A 1 appearing on the carry in line of a 1-bit adder cause it to generate a 1 on its carry out line. So, the carry signal propagate through the adder from right to left.
- The maximum signal propagation delay is  $nd$ , where  $d$  is the delay of a full-adder stage.
- The amount of hardware increase linearly with  $n$ .


# 2's Complement Adder-Subtractor

 

- When  $s = 0$ , then  $X \oplus s = X$
- When  $s = 1$ , then  $X \oplus s = \bar{X}$

# 2's Complement Adder-Subtractor

Example: Adder/Subtractor

 

# Overflow

- When the result of an arithmetic operation exceeds the standard word size  $n$ , overflow occurs.
- Example: let  $n=8$ ,  $X=11101011=235_{10}$  and  $Y=00101010=42_{10}$   
 $Z = X+Y = 11101011 + 0101010 = 00010101 = 21_{10}$   
with  $C_{n-1} = C_7 = 1$ .  
 $C_7Z = 100010101 = 277_{10} = 256_{10} + 21_{10}$
- The result of an addition simply wraps around when the largest number  $2^n-1$  is exceeded.
- For  $n$ , the number range for unsigned number is 0 to  $2^n-1$

# Overflow

- We can never have overflow on adding a negative and positive number.
- Example: let  $n=8$   $X=11101011=-21_{10}$  and  $Y=00101010=+42_{10}$   
 $Z = X+Y = 00010101 = 21_{10}$  and  $C_7 = 1$ .  
So,  $C_{n-1} = 1$  does not indicate overflow.
- Overflow in 2's complement addition can result from adding
  - 1) two positive numbers or
  - 2) two negative numbers.

# Overflow

Case 1: Two numbers are positive.

Let  $n = 4$ ,  $7 + 3 = 0111 + 0011 = 1010$  so,  $c_{n-2} = 1$

$C_{n-2} = 1$  indicates that the magnitude of the sum exceeds the  $n-1$  bits allocated to it.

Case 2: Two numbers are negative.

Let  $n=4$ ,  $-7 = 1001$ ,  $-3 = 1101$

so,  $1001 + 1101 = 10110$  so,  $c_{n-2} = 0$

$C_{n-2} = 0$  indicates the overflow.

# Overflow

$$Z_{n-1}Z_{n-2}\dots Z_0 := X_{n-1}X_{n-2}\dots X_0 + Y_{n-1}Y_{n-2}\dots Y_0$$

$$V = \overline{X_{n-1}}\overline{Y_{n-1}}C_{n-2} + \overline{X_{n-1}}Y_{n-1}\overline{C_{n-2}}$$

$$V = C_{n-1} \oplus C_{n-2}$$

$X_{n-1}$	$Y_{n-1}$	$C_{n-2}$	$Z_{n-1}$	$v$
0	0	0	0	0
0	0	1	0	1
0	1	0	1	0
0	1	1	0	0
1	0	0	1	0
1	0	1	0	0
1	1	0	1	1
1	1	1	1	0






# Carry-Lookahead Adder

- It reduce the time required to form carry signals.
- It computes the input carry needed by stage  $i$  directly from carrylike signals obtained from all the preceding stages  $i-1$ ,  $i-2$ , .....,  $0$ , rather than waiting for normal carries to ripple slowly from stage to stage.
- Adders that use this principle are called carry-lookahead adders.
 
# Carry-Lookahead Adder


- Two signals:  
generate signal,  $g_i = x_i y_i$   
propagate signal,  $p_i = x_i + y_i$
- $c_i = x_i y_i + x_i c_{i-1} + y_i c_{i-1}$
- $c_i = g_i + p_i c_{i-1}$
- $c_{i-1} = g_{i-1} + p_{i-1} c_{i-2}$
- $c_i = g_i + p_i g_{i-1} + p_i p_{i-1} c_{i-2}$



# 4-bit Carry-Lookahead Adder

- $c_i = g_i + p_i g_{i-1} + p_i p_{i-1} c_{i-2}$
- $c_0 = g_0 + p_0 c_{in}$   
 $c_1 = g_1 + p_1 g_0 + p_1 p_0 c_{in}$   
 $c_2 = g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_{in}$   
 $c_3 = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0 + p_3 p_2 p_1 p_0 c_{in}$
- $z_i = x_i \oplus y_i \oplus c_{i-1}$  can be written as  $z_i = p_i \oplus g_i \oplus c_{i-1}$

# 4-bit Carry-Lookahead Adder

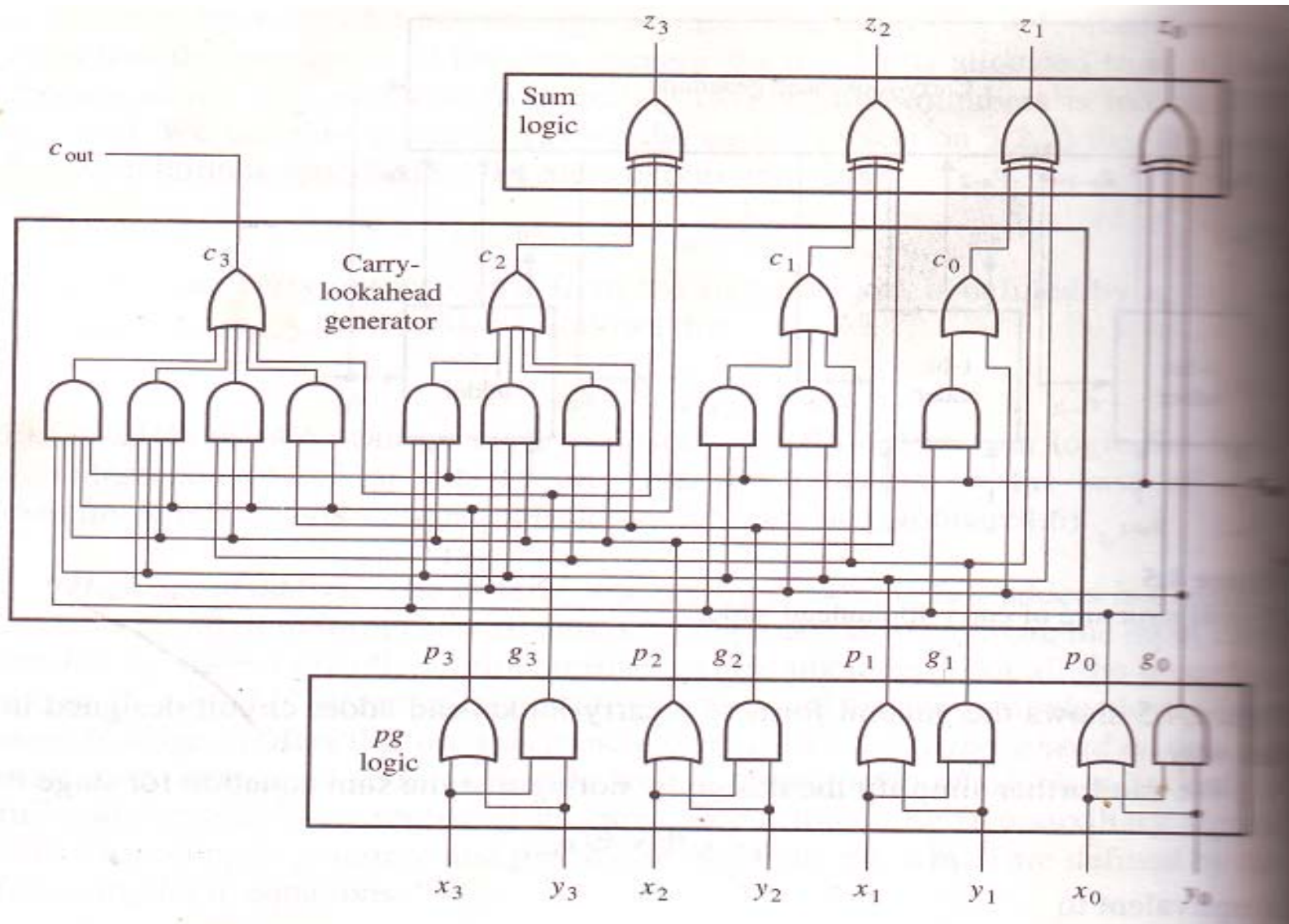


# 4-bit Carry-Lookahead Adder

- Maximum delay is  $4d$ , where  $d$  is the average gate delay. It is independent of number of input  $n$ .
- The number of gates grows in proportion to  $n^2$  as  $n$  increases.
- The complexity of the carry generation logic in the carry lookahead adder, including its gate count, its maximum fan-in, and its maximum fan-out, increase steadily with  $n$ .
- It limits  $n$  to 4.
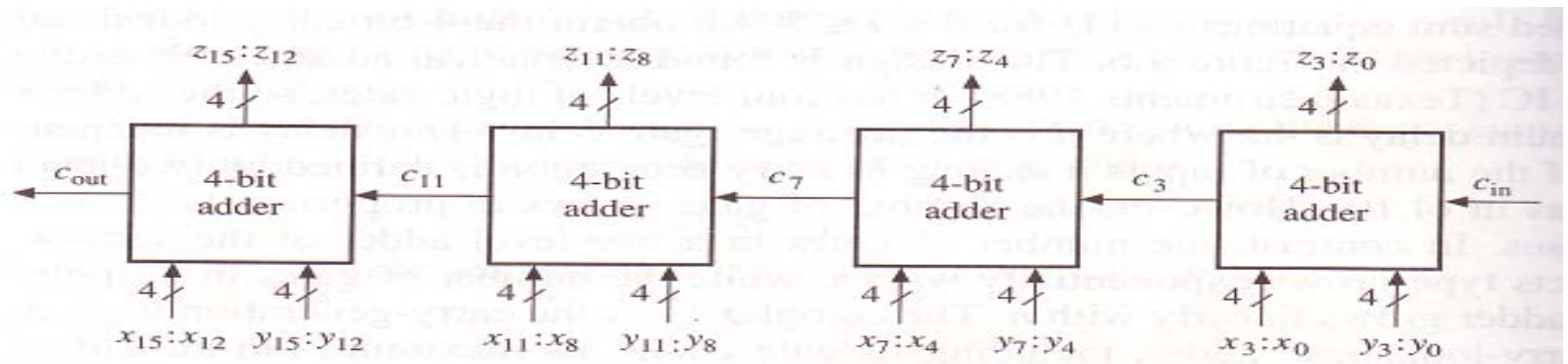
# Adder Expansion


- If we replace  $n$  1-bit adder stages in the  $n$ -bit ripple carry adder with  $n$   $k$ -bit adders, we obtain an  $nk$ -bit adder.



16-bit adder composed of 4-bit adders linked by ripple-carry propagation
 
# Adder Expansion

- If we replace  $n$  1-bit adder stages in the  $n$ -bit carry look-ahead adder with  $n$   $k$ -bit adders, we obtain an  $nk$ -bit adder.




16-bit adder composed of 4-bit adders linked by carry look-ahead

$$g = x_i y_i + x_{i-1} y_{i-1} (x_i + y_i) + x_{i-2} y_{i-2} (x_i + y_i) (x_{i-1} + y_{i-1})$$

$$+ x_{i-3} y_{i-3} (x_i + y_i) (x_{i-1} + y_{i-1}) (x_{i-2} + y_{i-2})$$


$$p = (x_i + y_i) (x_{i-1} + y_{i-1}) (x_{i-2} + y_{i-2}) (x_{i-3} + y_{i-3})$$
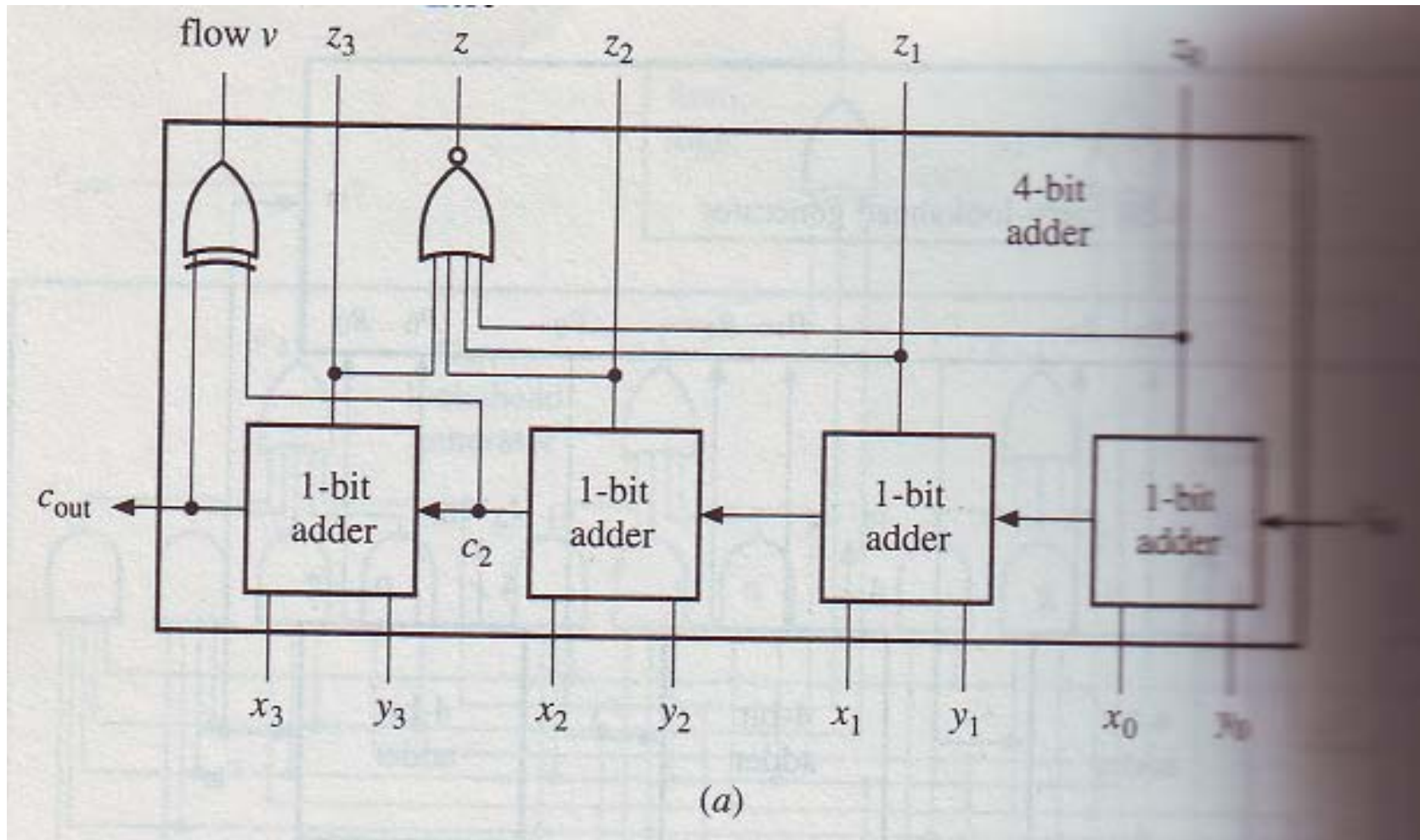
# Complete 2's Complement Adder-Subtractor





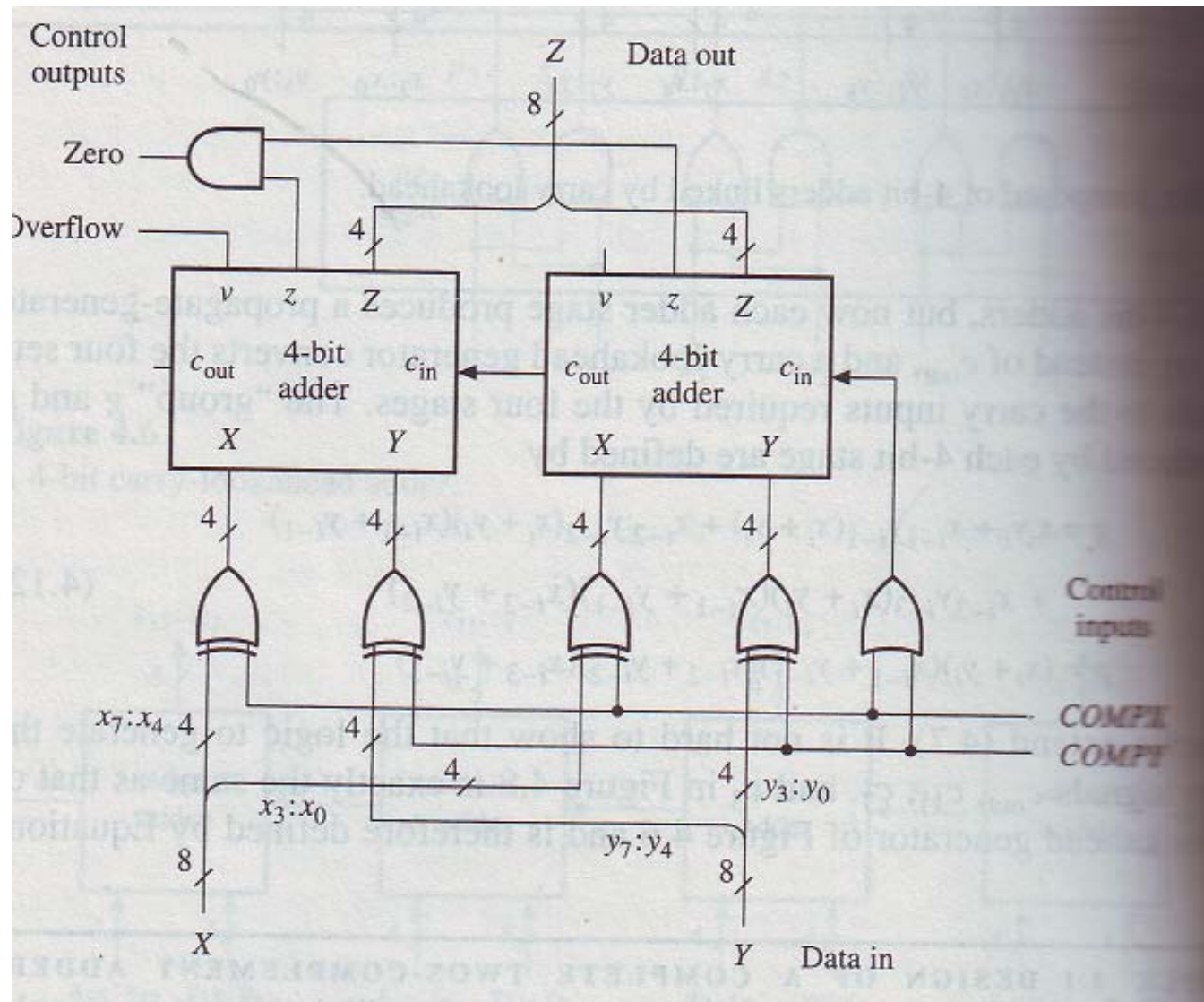
# Complete 2's Complement Adder-Subtractor



# Carry-Save Adder

 

# Carry-Save Adder

- One of the major speed enhancement techniques used in modern digital circuits is the ability to add numbers with minimal carry propagation.
- The basic idea is that three numbers can be reduced to 2, in a 3:2 compressor, by doing the addition while keeping the carries and the sum separate.

10111001

00101010

00111001

Sum: 10101010

Carry: 00111001

Result: 100011100

- The sum and carry can then be recombined in a normal addition to form the correct result.