

Understanding the ALU (Arithmetic Logic Unit)

Introduction

The **Arithmetic Logic Unit (ALU)** is a fundamental component of the CPU that performs all arithmetic and logical operations. It is a combinational digital circuit at the heart of all processors.

Main functions of the ALU:


- Arithmetic operations: addition, subtraction, increment, decrement.
- Logical operations: AND, OR, NOT, XOR.
- Comparison operations: equal, greater than, less than.
- Shift operations: left shift, right shift.

1 Basic ALU Architecture

An ALU takes two binary inputs and performs an operation based on control signals.

General Components

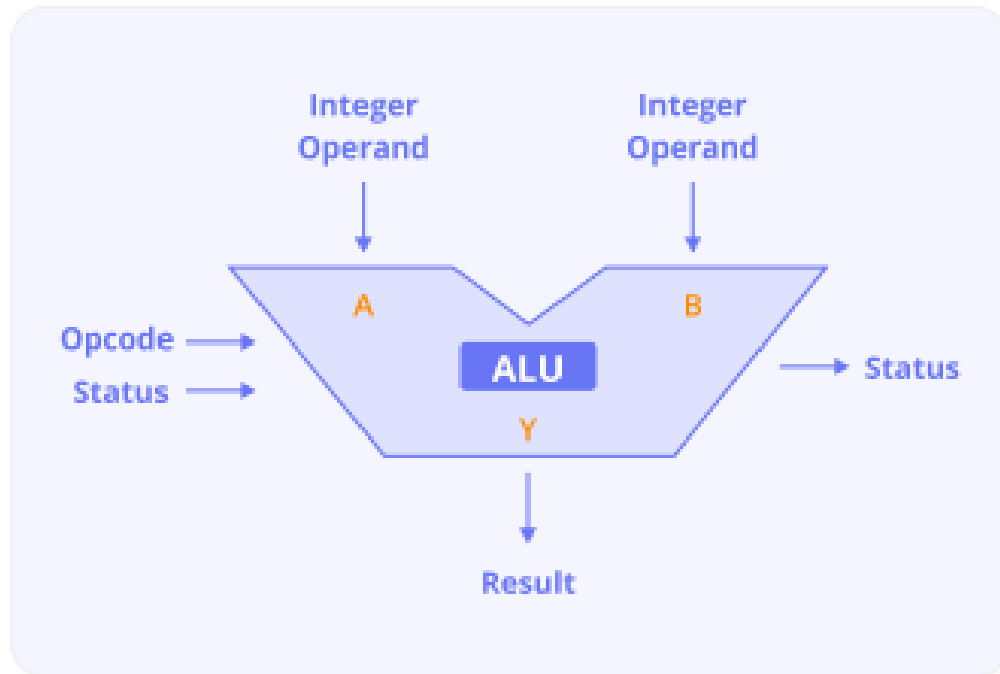- **Input operands:** A and B
- **Control signals:** Select operation
- **Operation circuitry:** Arithmetic and logic sub-units
- **Flags:** Zero, Carry, Overflow, Sign
- **Output:** Result



2 ALU Operations

2.1 Arithmetic Operations

- Addition: $R = A + B$
- Subtraction: $R = A - B$
- Increment: $R = A + 1$
- Decrement: $R = A - 1$

2.2 Logical Operations

- AND: $R = A \wedge B$
- OR: $R = A \vee B$
- XOR: $R = A \oplus B$
- NOT: $R = \sim A$

2.3 Comparison Operations

- Equal: $(A = B)$
- Greater than: $(A > B)$
- Less than: $(A < B)$

2.4 Shift Operations

- Logical Left Shift: $A \ll 1$
- Logical Right Shift: $A \gg 1$
- Arithmetic Right Shift: preserves sign bit


3 ALU Design Using Multiplexers

To create a compact ALU, we use multiplexers to select between operations.

Example: 1-bit ALU


A 1-bit ALU performs:

- AND
- OR
- ADD
- SUBTRACT

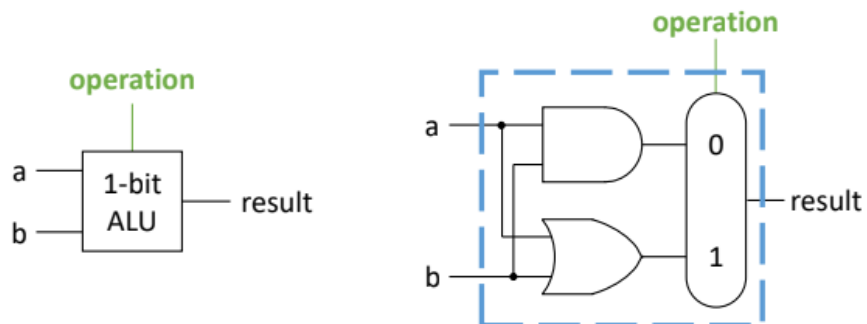


Example: N-bit ALU

N-bit ALU

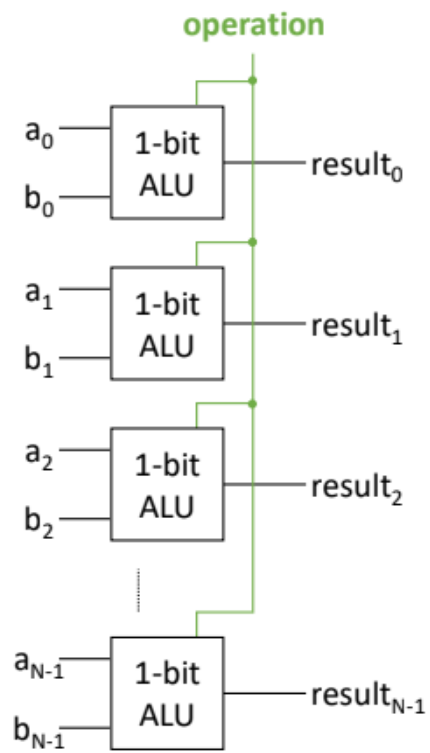


Example: Addition

1-bit ALU with Addition

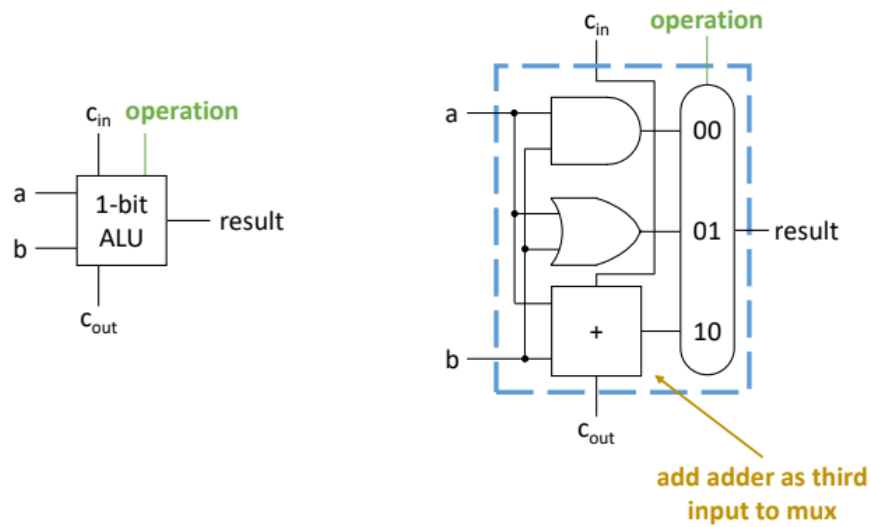


N-bit ALU with Addition

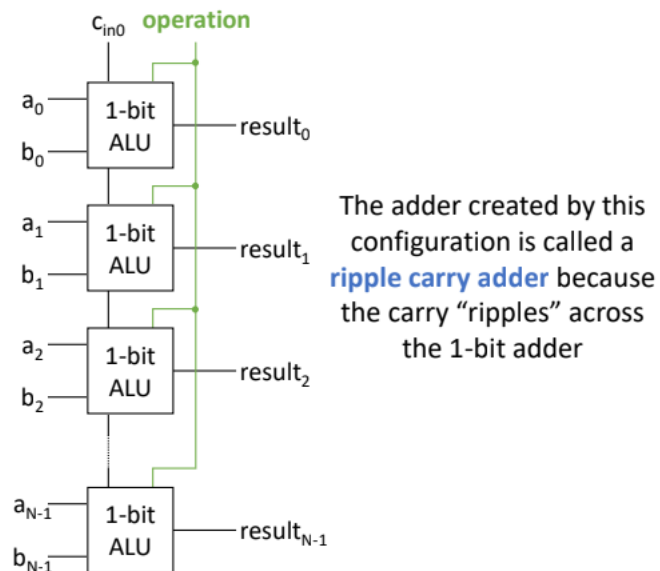


Example: Subtraction

1-bit ALU with Subtraction

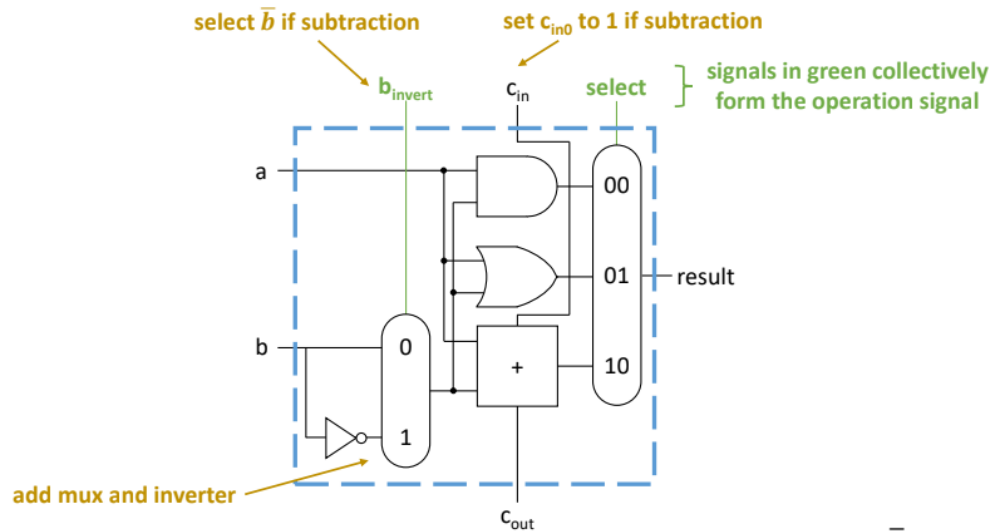


Example: NOR and NAND

1-bit ALU with NOR/NAND

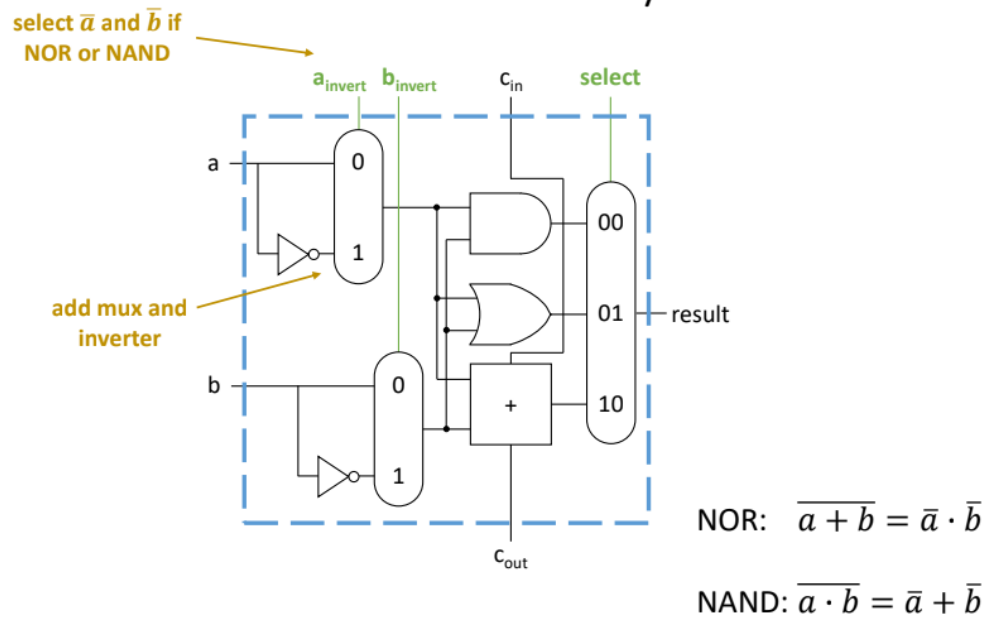


Example: Set on Less Than


1-bit ALU with SLT

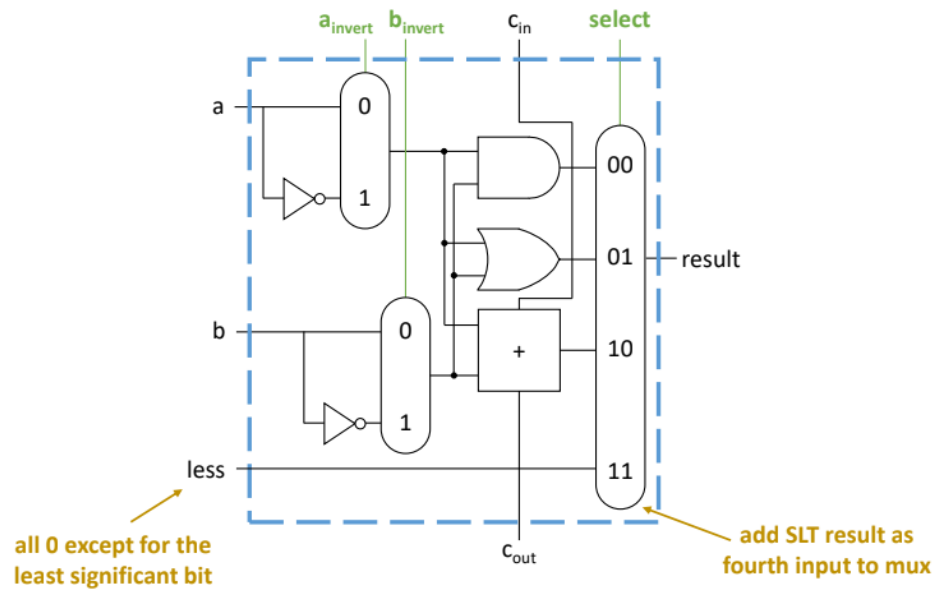

1-bit ALU for MSB with SLT

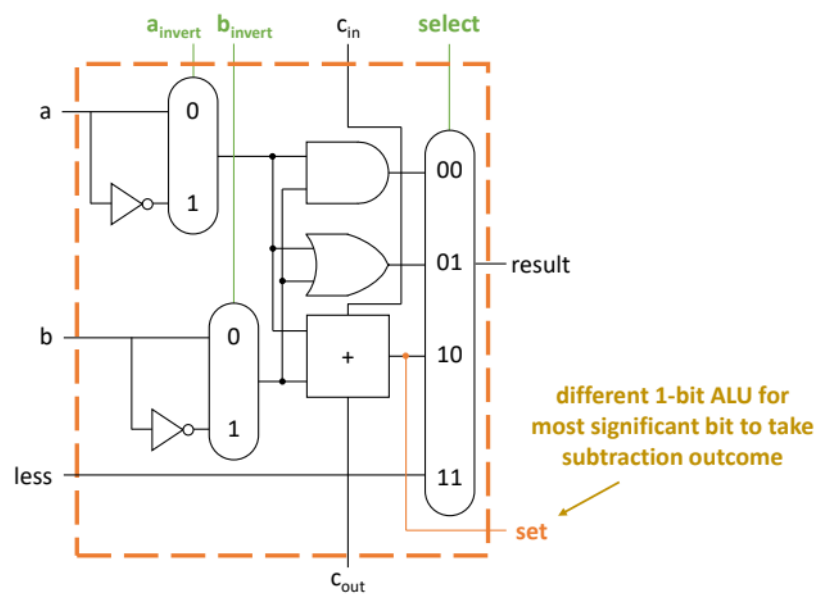


N-bit ALU with SLT

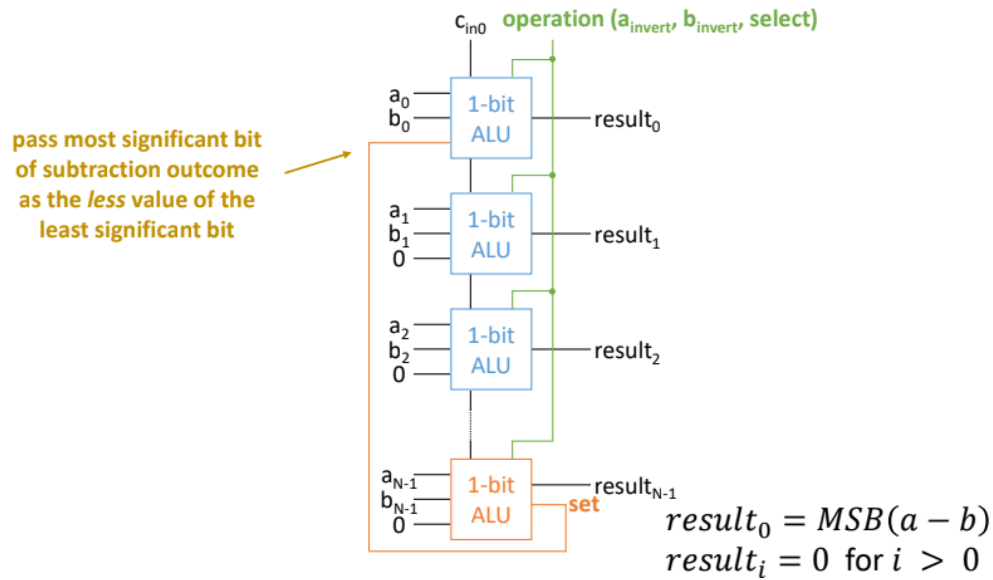


Example: Equality

N-bit ALU with Equality

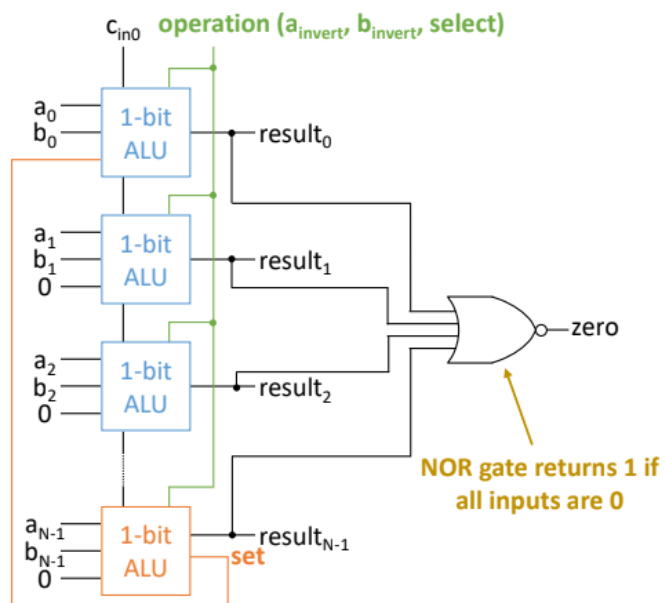


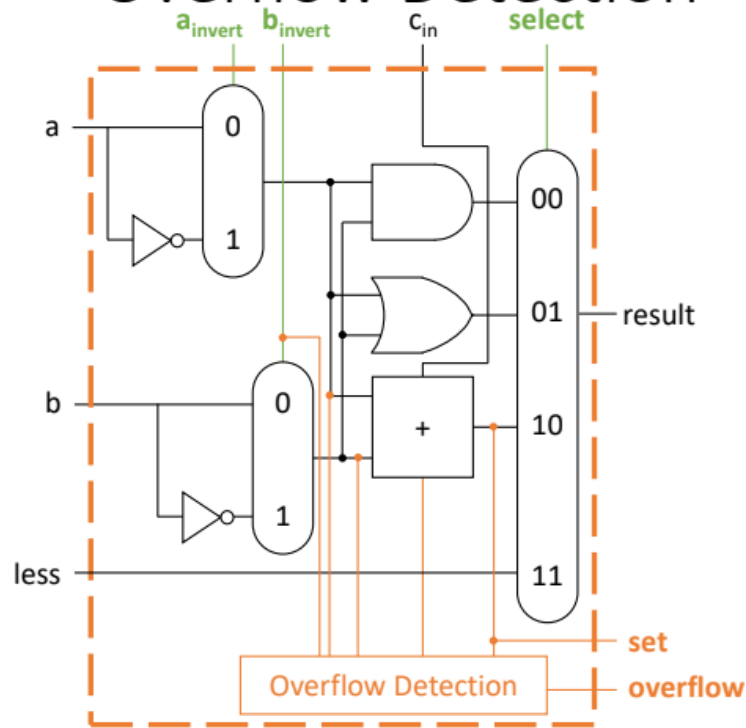Example: Overflow Detection

1-bit ALU for MSB with Overflow Detection



N-bit ALU with Overflow Detection

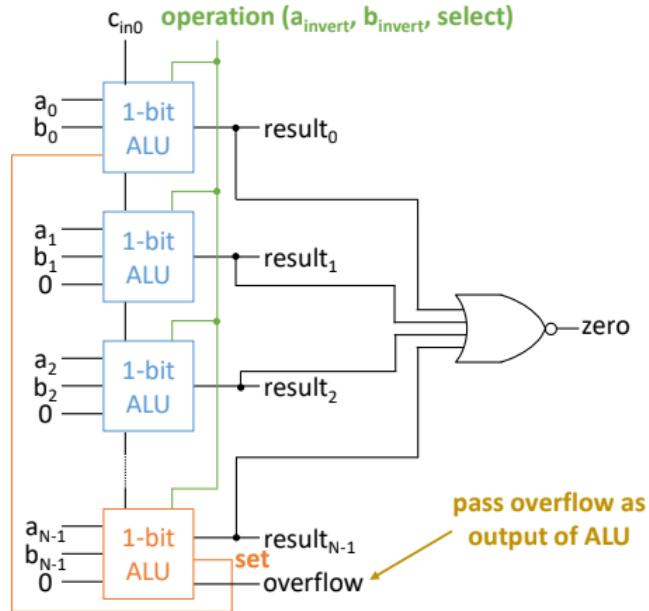

4 Status Flags

The ALU sets several status flags after an operation:

- **Zero (Z):** Result is zero
- **Carry (C):** Carry out of MSB in addition
- **Overflow (V):** Signed overflow occurred
- **Negative (N):** Result is negative (MSB = 1)

Flag	Description
Z	Zero result
C	Carry out
V	Signed overflow
N	Negative result

5 ALU Control Logic

The ALU control unit uses an opcode and function bits to select the correct operation.

Instruction opcode	ALUOp	Instruction operation	Func field	Desired ALU action	ALU control input
LW	00	load word	XXXXXX	add	0010
SW	00	store word	XXXXXX	add	0010
Branch equal	01	branch equal	XXXXXX	subtract	0110
R-type	10	add	100000	add	0010
R-type	10	subtract	100010	subtract	0110
R-type	10	AND	100100	and	0000
R-type	10	OR	100101	or	0001
R-type	10	set on less than	101010	set on less than	0111

6 Conclusion

The ALU is an essential building block of any computing system. Its ability to perform a variety of operations makes it the computational brain of the processor. Understanding ALU design and function is critical for comprehending processor architecture and digital logic design.