 


Lecture 12:

Multiplication Hardware


CMPS 221 – Computer Organization and Design

Last Time: Finite State Machines




Finite State Machine

 - A **finite state machine** (FSM) is a logic block consisting of inputs, outputs, and internal state
 - It includes an **output function** that computes the output from the inputs and current state
 - It includes a **next-state function** that computes a next state from the inputs and current state




- FSMs are used in computer architecture for building **controllers** which orchestrate a CPU's work, telling each of the other units what to do

Finite State Machine

 


Finite State Machine

 

FSM Example

 
- Example: a finite state machine that controls a traffic signal at an intersection



- Inputs:
 - **NSCar**: there is a car on the north-south road
 - **EWCar**: there is a car on the east-west road
- Outputs:
 - **NSLight**: turn the north-south light green
 - **EWLight**: turn the east-west light green

FSM Example

 - Example: a finite state machine that controls a traffic signal at an intersection



- Rules:
 - Rule #1: If a car is present on one road but not the other, turn green on the road where the car is
 - Rule #2: If a car is not present on either roads, stay green on the road that is currently green
 - Rule #3: If a car is present on both roads, turn green on the road that is not currently green

State Diagram

Inputs:

NSCar

EWCar

Outputs:


NSLight

EWLight


States:

NSGreen

EQGreen

 

Truth Table and Logic Equations

 

State _{current}	Outputs	
	NSLight	EWLight
0	1	0
1	0	1

State _{current}	Inputs		State _{next}
	NSCar	EWCAR	
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

Output Function:


$$NSLight = \overline{State_{current}}$$

$$EWLight = State_{current}$$

Next-State Function:

$$State_{next} = State_{current} \cdot NSCar + \overline{State_{current}} \cdot EWCAR$$

Logic Diagram

 

Output Function:


$$NSLight = \overline{State_{current}}$$

$$EWLight = State_{current}$$

Next-State Function:


$$State_{next} = State_{current} \cdot \overline{NSCar} + State_{current} \cdot EWCar$$

Today: Multiplication Hardware

 

Shift Registers

 - A **shift register** is an array of cascaded flip-flops sharing the same clock, where the output of one flip-flop is the input to the next flip-flop



- The resulting behavior is that the value stored in the register will shift by one position every cycle
 - Useful for implementing multiplication and division (and many other things)

Recall: Multiplication

Multiplicand:		1101
Multiplier:	×	1011

		1101
		1101
		0000
		1101

Product:		10001111

How to implement multiplication in hardware?

Implementing Multiplication

Multiplicand: 1101
Multiplier: × 1011

1101
1101
0000
1101

Product: 10001111



**product of two 4-bit operands
can have up to 8 bits
(use an 8-bit register for product)**

Implementing Multiplication

Multiplicand: 1101

Multiplier: × 1011

00001101

00011010

00000000

01101000

Product: 10001111

← multiplication of two 4-bit numbers can be
done as an addition of four 8-bit numbers
(use an 8-bit adder)

Implementing Multiplication

Multiplicand: 1101

Multiplier: × 1011

00001101

00011010

00000000

01101000


00000000

Product:

Implementing Multiplication

Multiplicand: 1101
Multiplier: × 1011

 00001101 →  ← 00000000
00011010 00001101
00000000
01101000



Product:

**addition of four 8-bit numbers
can be done as a sequence four
additions of two 8-bit numbers
(use an 8-bit adder with 2 inputs
4 times)**

Implementing Multiplication

Multiplicand: 1101
Multiplier: × 1011

00001101	→	+	←	00000000
00011010	→	+	←	00001101
00000000				00100111
01101000				

Product:

addition of four 8-bit numbers
can be done as a sequence four
additions of two 8-bit numbers
(use an 8-bit adder with 2 inputs
4 times)

Implementing Multiplication


Multiplicand: 1101
Multiplier: × 1011

00001101	→	+	←	00000000
00011010	→	+	←	00001101
00000000	→	+	←	00100111
01101000	→			00100111

Product:


addition of four 8-bit numbers
can be done as a sequence four
additions of two 8-bit numbers
(use an 8-bit adder with 2 inputs
4 times)

Implementing Multiplication

 


**addition of four 8-bit numbers
can be done as a sequence four
additions of two 8-bit numbers
(use an 8-bit adder with 2 inputs
4 times)**

Implementing Multiplication

 

rather than multiply multiplicand with 0
and add, simply use 0 to disable
updating the product with the sum

Implementing Multiplication

 

Overall approach:

- Shift **multiplicand** left on every cycle and add it to **product**
- Use **multiplier** bit to choose whether or not to update the **product** with the sum

Implementing Multiplication

Multiplicand: 1101
Multiplier: × 1011


00001101	→	+	←	00000000
00011010	→	+	←	00001101
00110100	→	+	←	00100111
01101000	→	+	←	00100111

10001111

Product:

Overall approach:

 - Shift **multiplicand** left on every cycle and add it to **product**
- Use **multiplier** bit to choose whether or not to update the **product** with the sum



Implementing Multiplication

Multiplicand:


1101

Multiplier:

×

1011

Cycle 0:

 


Product:

10001111

Overall approach:

 - Shift **multiplicand** left on every cycle and add it to **product**
- Use **multiplier** bit to choose whether or not to update the **product** with the sum




Implementing Multiplication

Multiplicand: 1101
Multiplier: × 1011

Cycle 0: 00001101 → + → 00000000
Cycle 1: 00011010 → + → 00001101
00110100 → + → 00100111
01101000 → + → 00100111
Product: 10001111

Overall approach:

 
- Shift **multiplicand** left on every cycle and add it to **product**
- Use **multiplier** bit to choose whether or not to update the **product** with the sum



Implementing Multiplication


Multiplicand: 1101

Multiplier: × 1011

 

Overall approach:

 
- Shift **multiplicand** left on every cycle and add it to **product**
- Use **multiplier** bit to choose whether or not to update the **product** with the sum



Implementing Multiplication


Multiplicand: 1101

Multiplier: $\times$ 1011

 

Overall approach:

 - Shift **multiplicand** left on every cycle and add it to **product**
- Use **multiplier** bit to choose whether or not to update the **product** with the sum



Implementing Multiplication

Multiplicand: 1101

Multiplier: × 1011


Cycle 0: 00001101 → + ← 00000000
Cycle 1: 00011010 → + ← 00001101
Cycle 2: 00110100 → + ← 00100111
Cycle 3: 01101000 → + ← 00100111

Product:

10001111


Overall approach:

 - Shift **multiplicand** left on every cycle and add it to **product**
- Use **multiplier** bit to choose whether or not to update the **product** with the sum




Cost of N -bit Multiplication

 - Cost:
 - ALU: $2N$
 - Registers: $5N$
 - Time: N
- Can we do better?
 - Use less hardware?
 - Finish faster?




Multiplication with Less Hardware

 


**only 4 bits of the
multiplicand are useful**
(the rest are always zero and
do not need to be stored)

Multiplication with Less Hardware

 



Multiplication with Less Hardware

 

Overall approach:

- Shift product window left (shift **product** right) on every cycle and add it to the stationary **multiplicand**
- Use **multiplier** bit to choose whether or not to update the **product** with the sum

Multiplication with Less Hardware

  

Overall approach:

- Shift product window left (shift **product** right) on every cycle and add it to the stationary **multiplicand**
- Use **multiplier** bit to choose whether or not to update the **product** with the sum

Multiplication with Less Hardware

Multiplicand:


1101

Multiplier:

×

1011

Cycle 0:

 


Product:

10001111

Overall approach:

 
- Shift product window left (shift **product** right) on every cycle and add it to the stationary **multiplicand**
- Use **multiplier** bit to choose whether or not to update the **product** with the sum



Multiplication with Less Hardware

Multiplicand: 1101
Multiplier: × 1011

Cycle 0:

 


Product:

10001111


Overall approach:

 - Shift product window left (shift **product** right) on every cycle and add it to the stationary **multiplicand**
- Use **multiplier** bit to choose whether or not to update the **product** with the sum



Multiplication with Less Hardware


Multiplicand: 1101
Multiplier: × 1011

 

Multiplication with Less Hardware

Multiplicand: 1101
Multiplier: x 1011

Cycle 0:

 


Product:

10001111

Overall approach:

 - Shift product window left (shift **product** right) on every cycle and add it to the stationary **multiplicand**
- Use **multiplier** bit to choose whether or not to update the **product** with the sum



Multiplication with Less Hardware

Multiplicand: 1101

Multiplier: × 1011

Cycle 0:

0000	1101	→	+	←	00000000	
000	1101	0	→	+	←	00001101
00	1101	00	→	+	←	00100111
0	1101	000	→	+	←	00100111


Vertical multiplier bits (1, 1, 0, 1) are shown to the left of the adders. A red 'X' is over the third adder (multiplier bit 0). Arrows indicate the shift of the multiplicand into the adders.

Product:

10001111

Overall approach:

 - Shift product window left (shift **product** right) on every cycle and add it to the stationary **multiplicand**
- Use **multiplier** bit to choose whether or not to update the **product** with the sum



Can we do even better?

Let's replay and see...

Multiplication with Less Hardware

Multiplicand:


1101

Multiplier:

×

1011

Cycle 0:

 


Product:

10001111

Overall approach:

 - Shift product window left (shift **product** right) on every cycle and add it to the stationary **multiplicand**
- Use **multiplier** bit to choose whether or not to update the **product** with the sum




number of unused bits in product register is the same as the number of used bits in multiplier register

Multiplication with Less Hardware

Multiplicand: 1101
Multiplier: × 1011

Cycle 0:

 


Product:

10001111

Overall approach:

 - Shift product window left (shift **product** right) on every cycle and add it to the stationary **multiplicand**
- Use **multiplier** bit to choose whether or not to update the **product** with the sum




number of unused bits in product register is the same as the number of used bits in multiplier register

Multiplication with Less Hardware

Multiplicand: 1101
Multiplier: × 1011

Cycle 0:

 


Product:

10001111

Overall approach:

 - Shift product window left (shift **product** right) on every cycle and add it to the stationary **multiplicand**
- Use **multiplier** bit to choose whether or not to update the **product** with the sum



number of unused bits in product register is the same as the number of used bits in multiplier register

Multiplication with Less Hardware

Multiplicand: 1101
Multiplier: 1011


Cycle 0:

0000	1101	→	+	←	00000000	
000	1101	0	→	1	←	00001101
00	1101	00	→	1	←	00100111
0	1101	000	→	0	←	00100111
	1101	000	→	1	←	00100111

Product: 10001111

Overall approach:

 - Shift product window left (shift **product** right) on every cycle and add it to the stationary **multiplicand**
- Use **multiplier** bit to choose whether or not to update the **product** with the sum




number of unused bits in product register is the same as the number of used bits in multiplier register

Multiplication with Less Hardware

Multiplicand: 1101

Multiplier: × 1011

Cycle 0:

 


Product:

10001111

Overall approach:

 - Shift product window left (shift **product** right) on every cycle and add it to the stationary **multiplicand**
- Use **multiplier** bit to choose whether or not to update the **product** with the sum



number of unused bits in product register is the same as the number of used bits in multiplier register

Optimization: reuse the same
register for multiplier and lower
half of product

Let's replay again and see...

Multiplication with Less Hardware

Multiplicand:


1101

Multiplier:

×

1011

Cycle 0:

 


Product:

10001111

Overall approach:

 
- Shift product window left (shift **product** right) on every cycle and add it to the stationary **multiplicand**
- Use **multiplier** bit to choose whether or not to update the **product** with the sum



Multiplication with Less Hardware

Multiplicand: 1101
Multiplier: × 1011

Cycle 0:

 


Product:

10001111

Overall approach:

 
- Shift product window left (shift **product** right) on every cycle and add it to the stationary **multiplicand**
- Use **multiplier** bit to choose whether or not to update the **product** with the sum



Multiplication with Less Hardware

Multiplicand: 1101
Multiplier: × 1011

Cycle 0:

 


Product:

10001111

Overall approach:

 - Shift product window left (shift **product** right) on every cycle and add it to the stationary **multiplicand**
- Use **multiplier** bit to choose whether or not to update the **product** with the sum




Multiplication with Less Hardware

Multiplicand: 1101

Multiplier: x 1011

Cycle 0:

 


Product:

10001111

Overall approach:

 - Shift product window left (shift **product** right) on every cycle and add it to the stationary **multiplicand**
- Use **multiplier** bit to choose whether or not to update the **product** with the sum




Multiplication with Less Hardware

Multiplicand: 1101

Multiplier: × 1011


Cycle 0:

 

Product:


Overall approach:

 - Shift product window left (shift **product** right) on every cycle and add it to the stationary **multiplicand**
- Use **multiplier** bit to choose whether or not to update the **product** with the sum



Cost of N -bit Multiplication

 - First design:
 - ALU: $2N$
 - Registers: $5N$
 - Time: N
- Second design:
 - ALU: N
 - Registers: $3N$
 - Time: N
- Can we do better?
 - Finish faster?




Multiplication Faster


Multiplicand: 1101
Multiplier: × 1011

00001101
00011010
00000000
01101000

Multiplication Faster

 


Multiplication Faster

 

Multiplication Faster


Multiplicand: 1101
Multiplier: × 1011

 00001101
00011010 → + → 00100111
00000000
01101000 → + → 01101000 → + → **Product: 10001111**



Cost of N -bit Multiplication

 - First design:
 - ALU: $2N$
 - Registers: $5N$
 - Time: N
- Second design:
 - ALU: N
 - Registers: $3N$
 - Time: N
- Third design:
 - ALU: $N \times (N-1)$
 - Time: $\log_2 N$



Textbook Sections

- Some of the content in these slides corresponds to:
 - Textbook:
 - *Computer Organization and Design, 5th Edition by David Patterson and John Hennessy, Morgan Kaufmann, 2014.*
 - Sections:
 - 3.3